Half Adder



Α	В	Cout	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{array}{ll} S &= A \oplus B \\ C_{out} &= AB \end{array}$$